

## Report on Multipliers

-- Chelsi Raheja 16CS10013

-- Mehul Nirala 16CS10034

### Unsigned Array Multiplier:

Speed of Operation: Maximum combinational path delay: 42.267ns

Hardware Requirement:

1-bit adder carry out : 64

2-bit adder : 64

### Combinational Multiplier:

Speed of Operation: Maximum combinational path delay: 46.918ns

Hardware Requirement:

1-bit adder carry out : 64

16-bit adder : 1

2-bit adder : 64

8-bit adder : 2

1-bit xor2 : 1

\*\* Additional delay and hardware is because of using multiplexers and complements for signed numbers\*\*

### Booth Multiplier:

Speed of Operation:

Minimum input arrival time before clock: 4.311ns

Maximum output required time after clock: 7.773ns

Hardware Requirement:

1-bit adder carry out : 12

2-bit adder : 12

4-bit up counter : 1

1-bit register : 7

6-bit register : 2

1-bit 4-to-1 multiplexer : 1

6-bit 4-to-1 multiplexer : 1

**Conclusion:** Booth Multiplier requires way less hardware than combinational multiplier and computation power required is very less compared to combinational but output depends on the clock speed.

